

Daniel Leeds, 6.004 R10, March 15, 2006; Quiz #2 Review

**Fine print:**

Quiz is closed-book, no calculators; covers up to L09 (Pipelining)/R10 (this recitation)

**Practice, practice, practice:**


Follow “Previous terms” link from <http://6004.csail.mit.edu>, pick a semester (the more recent, the better), click on the “Announcements” page for the semester, and find the PDF for Quiz 2 solutions. (For semesters from a few years ago, some (or all) of the material may be in Quiz 1.) Don’t read the answers until you first figure them out for yourself!

**Another perspective on the material – Margaret Chong’s Handbook:**

Follow “Handouts” link from <http://6004.csail.mit.edu>, click on handbook link near the bottom of the page.

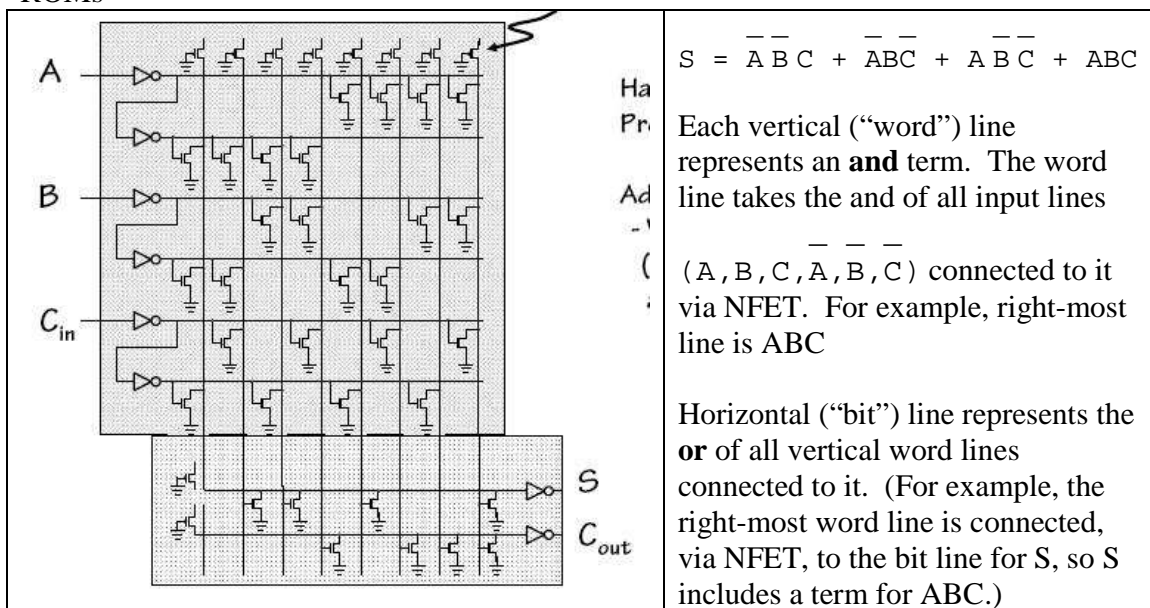**Good topics to know:**

*Synthesis of Combinational Logic*  
ROMs



**Karnaugh Maps**

“A truth table arranged so that terms which differ by exactly one variable are adjacent to one another”

Strategy (circling the 1s):

Circle largest N-dimensional rectangles (with sides of  $2^N$ )

Keep circling largest remaining rectangles (even if they overlap) until no 1s are left

Choose fewest rectangles to cover all the ones -> Minimal SOP form


Include terms for all prime implicants to construct a lenient circuit.

### Sequential Logic

Our registers latch in new value at rising clock edge

$t_{\text{SETUP},R1}$  and  $t_{\text{HOLD},R1}$  must be met by R1's input to guarantee valid output at R1

 $t_{\text{CD},R1}$  and  $t_{\text{PD},R1}$  relate to R1 output after clock edge



$$t_{\text{HOLD},R2} < t_{\text{CD},R1} + t_{\text{CD},CL}$$

$$t_{\text{CLK}} > t_{\text{SETUP},R2} + t_{\text{PD},R1} + t_{\text{PD},CL} \leftrightarrow t_{\text{SETUP},R2} < t_{\text{CLK}} - (t_{\text{PD},R1} + t_{\text{PD},R2})$$

### FSMs

A Finite State Machine consists of  $k$  states. Each state has a set of transition rules for each input, and may have one or many outputs.

Hardware Implementation

ROM-register loop

$2^n$  states,  $m$  inputs,  $p$  outputs  $\rightarrow p \cdot 2^{(n+m)}$  bits in ROM (i.e., output entries in FSM truth table)

### Synchronization/Metastability

Time-based problem – inputs occur too close together in time (asynchronous inputs)

Metastable state resolves in **unbounded** time

“Solution:” Cascading flip-flops increases the probability that the metastable state will be resolved to valid logic value before our logic circuitry sees it.

Alternative “solution:” realize you are supposed to be using combinational logic.

Combinational logic has valid output in bounded time.

### Pipelining

Typically, better performance means:

decreasing latency and/or  
increasing throughput

Pipelines:

**can** increase throughput (not always)

**may** increase latency (not always)

Un-pipelined circuit: Latency = 1 / Throughput

In pipelined circuit: Latency = (# pipeline stages) \* ( $t_{\text{PD}}$  at longest pipeline stage)

Methodology:

1 Draw a line that crosses every output in the circuit and mark the endpoints as terminal points.

2 Continue to draw new “separating lines” between the terminal points across various circuit connections; add a pipeline register at every point where a separating line crosses a connection in the circuit.

Can place multiple registers between two circuit components, but each register must be part of a separate pipeline stage.

Circuit Interleaving: Interleaving  $n$  copies of a device increases throughput  $n$ -fold.

Pipelining starting with ibm 7094 circa 1969

