

Array-Based Architecture for Molecular Electronics

André DeHon
<andre@cs.caltech.edu>



DeHon February 2002

Molecular Scale Building Blocks

- Chemists starting to demonstrate
 - Molecular-scale switching devices
 - Molecular-scale wires
 - Regular assembly techniques for these components

DeHon February 2002


Computing?

- **Problem:** How can we build computing devices from this technology?
 - Organize into useful connectivity?
 - Provide signal restoration?
 - Personalize/Engineer to perform specific computation?
 - Accommodate defects?

DeHon February 2002

Architecture Goal

 - This talk:
 - Starting with these building blocks
 - Show how to build universal, programmable computing array.



DeHon February 2002


Outline

- Review Components
- Restoring Logic Style
- Bootstrap Programming
- Routing
- Defect Tolerance
- Summary

DeHon February 2002

Wires


SWNT (Single Wall Carbon Nanotubes)

 

- Nanometer(s) diameter
- microns long
- good conductors

SiNW (Silicon Nanowires)


- Dope to control electrical properties

 


DeHon February 2002

Devices

Diode and FET Junctions

 

Electrostatic Switches

 

DeHon February 2002

Unique Characteristics

- Can only build very regular structures at nanoscale
 - Arrays of crossed tubes / wires
- Will have many defects
- Can store state of switch in wire crossing
 - Contrast with VLSI where switch \gg wire xing
- Switching occurs at tube/wire crossing
 - Not at substrate...long term 3D opportunity


DeHon February 2002

Strategy


DeHon February 2002

Strategy

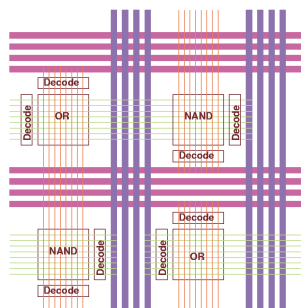- Arrays of FETs for gain
- FET decode for bootstrap program
- PLA logic in arrays
- Overlapping wires for interconnect



DeHon Feb

 


Logic Discipline

DeHon February 2002

Diode Logic

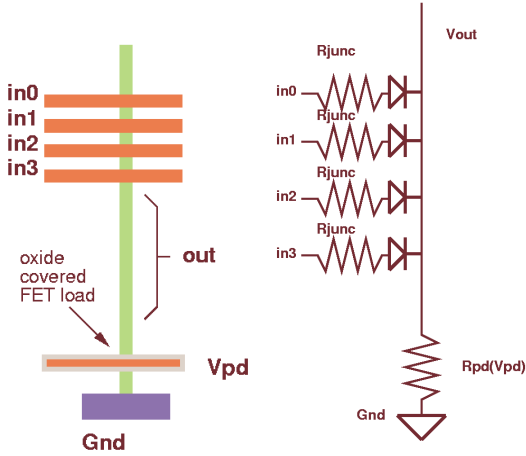
- Arise directly from touching NW/NTs
- Passive logic
- Non-restoring



DeHon February 2002

PMOS-like Restoring FET Logic

 
- Use FET connections to build restoring gates
- Static load
 - Like NMOS (PMOS)



DeHon February 2002

PMOS-like Logic

 
$$V_{out} = V_{dd} \left(\frac{R_{pd} + R_c}{R_c + \sum_{i=0}^{M-1} (R_{pfet}(V_i)) + R_{pd} + R_c} \right)$$



DeHon February 2002

Operating Point

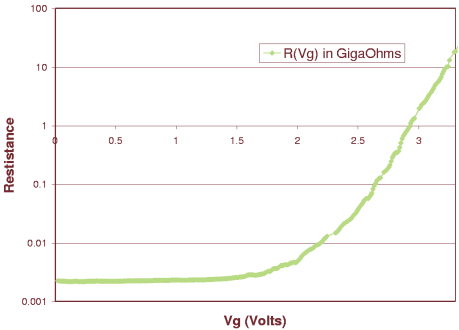
$$V_{out} = V_{dd} \left(\frac{R_{pd} + R_c}{R_c + \sum_{i=0}^{M-1} (R_{pfet}(V_i)) + R_{pd} + R_c} \right)$$



V_{dd}	3.3V
V_{oh}	3.0V
V_{ih}	2.8V
V_{il}	0.5V
V_{ol}	0.15V
V_{pd}	2.4V

DeHon February 2002

Programmed FET Arrays

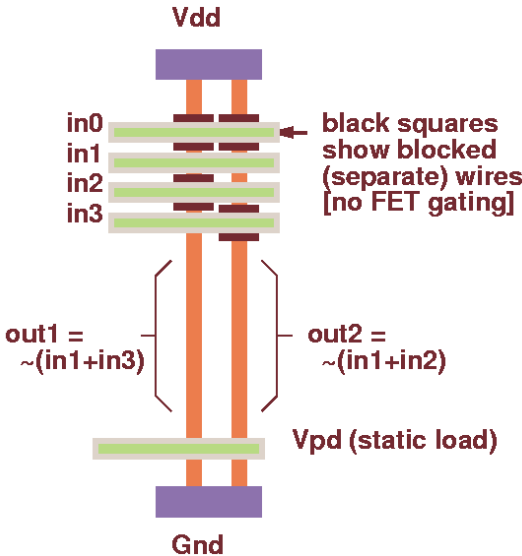

DeHon February 2002


Interfacing and Programming

Micro→nanoscale

DeHon February 2002

FET Decoders

 - FETs also ideal for decoding/drive at nano-micro interface



DeHon February 2002

Program Decoder


- Will need to program the decoder
 - Different scheme; in fabrication
 - Imprinting/stamping



DeHon February 2002

Operating Array

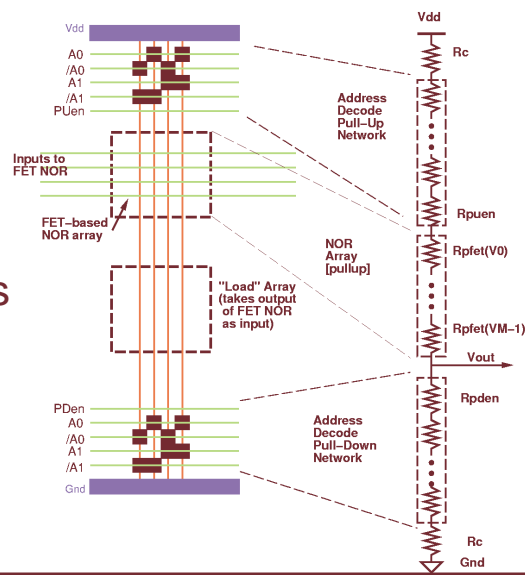
- Decoders allow program array
 - OR, NOR
- Isolatable
- Dual role of loads during operation
- Output used directly by consumer



DeHon February 2002

Assembly

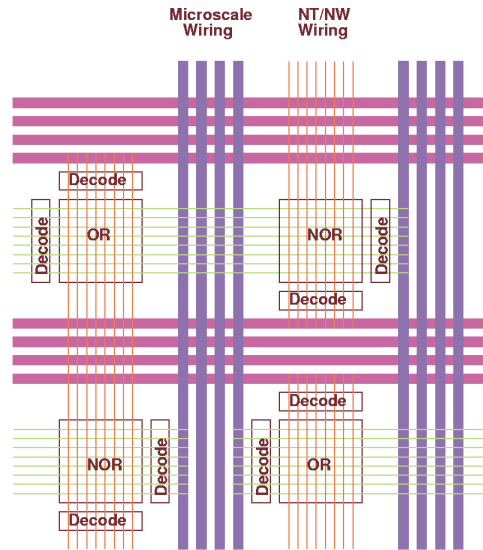
- Overlapping NW/NT between arrays provide interconnect
- NOR only sufficient
- Alternate:
 - Programmable (non-restoring) OR
 - followed by fixed (restoring) NOR



DeHon February 2002


Routing

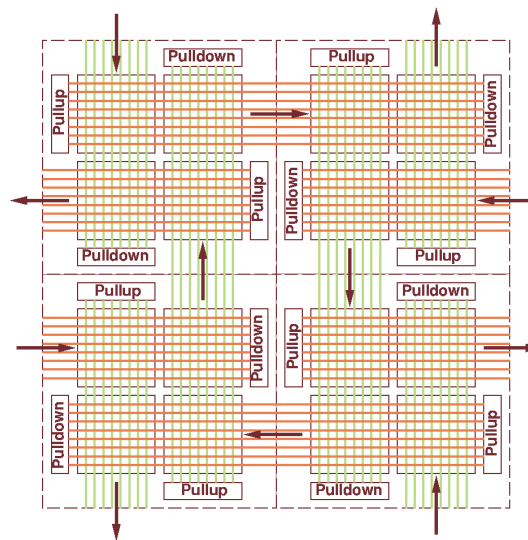- X-Y, mesh routing with appropriate tile overlap




DeHon February 2002

Defect Tolerance

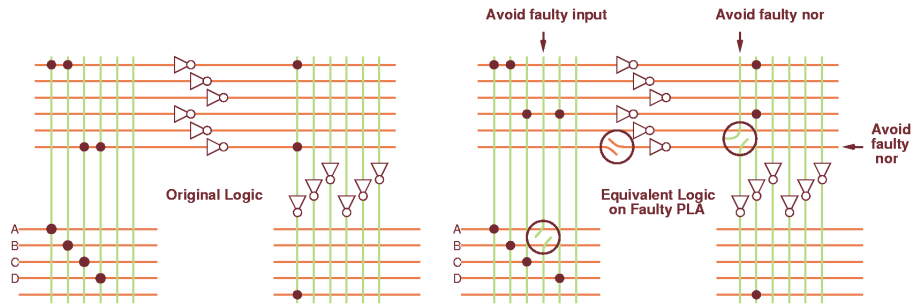

All components (PLA, routing) interchangeable;
Allows local programming around faults

DeHon February 2002

 

Summary

- Universal, Programmable Architecture
 - Built entirely from large arrays of crossed NT/NWs
- Provides restoration and inversion entirely at nanoscale
- Support nanoscale bootstrap programming
- Designed to tolerate defective components

DeHon February 2002