

# A Potentially Implementable FPGA for Quantum-Dot Cellular Automata

Michael T. Niemier, University of Notre Dame


Arun Rodrigues, University of Notre Dame

Peter Kogge, University of Notre Dame


Special Thanks to: NSF



University of Notre Dame

 


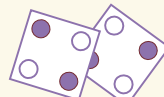
## Motivation

- **A Problem: CMOS Limitations**
  - Moore's Law: 2x transistor gain every 3 years in CMOS
  - Moore's Law Obstacles: Dopants, quantum effects, \$\$\$
- **A Solution: QCA**
  - QCA = another way to do computation – but quantumly
  - QCA device = 4 quantum dots positioned in a square
- **A Design Target: A QCA FPGA**
  - Previous designs have been "custom" 
  - Near term focus: not the fastest, densest circuit
  - Instead, develop work for implementation experiment.
  - Simple, regular structures are desired (as they might target best for self-assembly)




University of Notre Dame

## Where we've been





**Early QCA work mainly devices**

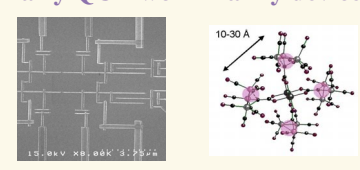


10-30 Å

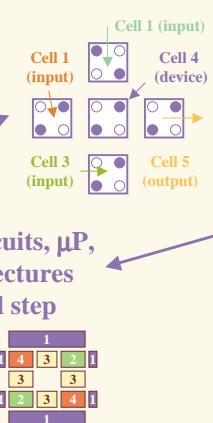**Simple circuits,  $\mu$ P, and architectures next logical step**




Cell 1 (input), Cell 3 (input), Cell 4 (device), Cell 5 (output)

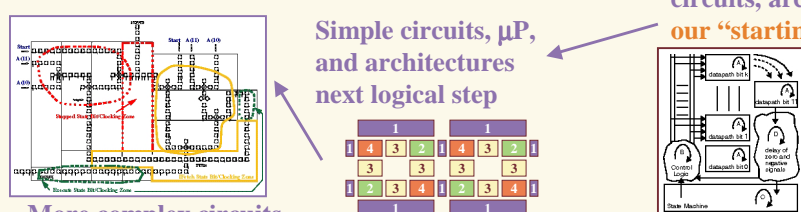**More complex circuits, control logic, and  $\mu$ Architecture work followed**




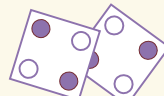
**Progressed to simple circuits, architectures – our "starting point"**

Now, we move on to something that can be built in near-term




University of Notre Dame

## The Basics

### The Device

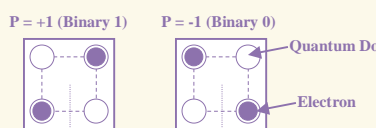


P = +1 (Binary 1)    P = -1 (Binary 0)

Quantum Dot

Electron

Proposed experiment – 42 nm  
Future molecular – 4.2 nm  
(and room temperature)


### Wire Cross in the Plane

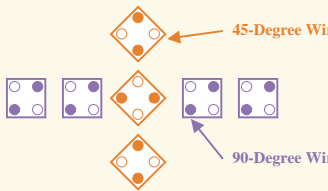

45-Degree Wire

90-Degree Wire

### A 45-degree Wire

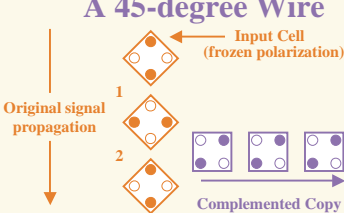


Input Cell (frozen polarization)

Original signal propagation


Complemented Copy

### A QCA Wire

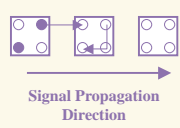


Signal Propagation Direction

### Majority Gate

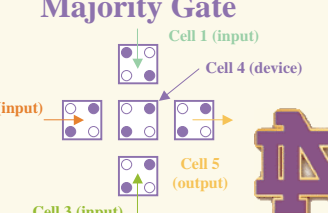



Cell 1 (input), Cell 3 (input), Cell 4 (device), Cell 5 (output)



University of Notre Dame



# Experimental QCA

  

- Early and present work uses “metal” dots
- Low temperatures – 70 mK


A. Orlov, I. Amlani, G. Bernstein, C. Lent, G. Snider, "Realization Of a functional cell for quantum-dot cellular automata." Science, 277:928-930, 1997.

## • QCA wire demonstrated





A. Orlov, I. Amlani, C. Lent, G. Bernstein, G. Snider, "Experimental demonstration of a binary wire for quantum-dot cellular automata." Applied Physics Letters, 74: 2875-77, 1999.

## • QCA with chemical molecules

 



C. Lent, "Molecular electronics: Bypassing the transistor paradigm." Science, 288:1597-1599, 2000.
  
## • 3-input majority logic gate demonstrated



I. Amlani, A. Orlov, G. Toth, G. Bernstein, C. Lent, G. Snider, "Digital logic gate using quantum-dot cellular automata." Science, 284: 289-291, 1999.

## • Single-bit memory demoed

  


A. Orlov, R. Kumamuru, R. Ramasubramanian, G. Toth, C. Lent, G. Bernstein, G. Snider, "Experimental demonstration of a latch in Clocked quantum-dot cellular automata: Review and recent Experiments." J. of Appl. Physics, 85: 4283-85, 1999

## • Clocked QCA cells demonstrated


- Power gain demoed
- Work underway to raise operating temp.



# FPGA Properties

 


- Generically, an FPGA = a collection of functionally complete logic elements arranged in some interconnection framework
- A common, unique feature is a pattern of horizontal and vertical wires with programmable connections for data routing...
- Logic blocks can be connected directly – direct interconnection...
- ...or via long-line interconnect wires that bypass logic blocks to move a signal “far away”

 



# The QCA Clock

 


## The CMOS Clock

- ✓ The standard CMOS clock is signal controlling memory transfers
- ✓ The CMOS clock is 2 phases


## The QCA Clock

- ✓ QCA clock not a wire or port
- ✓ QCA “clock” an E-field controlling barriers, suppressing e<sup>-</sup> tunneling
- ✓ E-field = 4 phase clock

## The QCA Clock Phases

 

 - ✓ Cells begin unpolarized
- ✓ Barriers raised, cells “latched”



- ✓ Barriers are held high
- ✓ Used as input to next zone





- ✓ Barriers are lowered
- ✓ Cells relax to unpolarized state



- ✓ Cell barriers remain lowered
- ✓ Unpolarized, neutral state stays




# A Clocking Example

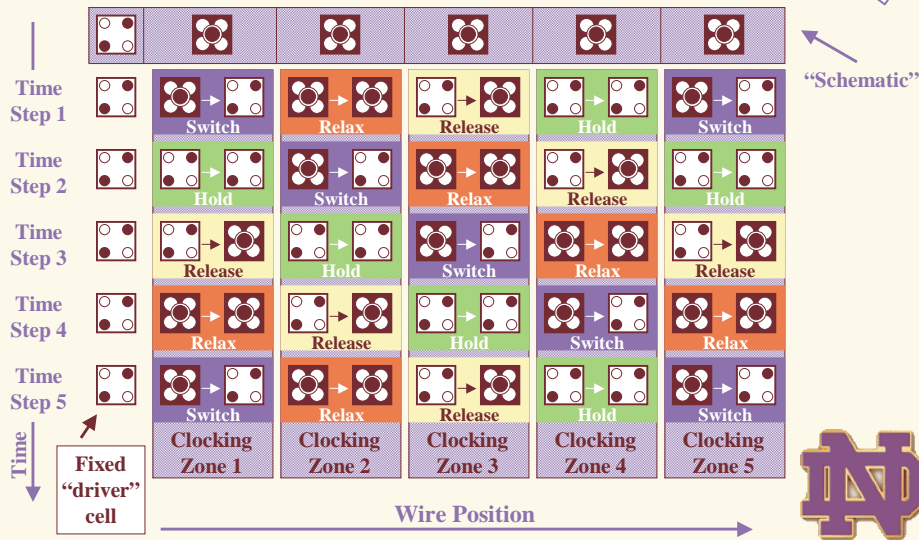 




## FPGAs in QCA

 

 
- The QCA clock scheme results in “inherent self latching” for data movement (i.e. a shift register)
- Information transmission is “pipelined” and not instantaneous (unlike CMOS electron flow)
- Must coordinate arrival times of signals to logic
- Alternative: One big wire in one big clocking zone




- Why the alternative doesn't work:
  - As a QCA wire grows in length, the probability that all cells will switch successfully decreases



## Switching Matrices and QCA

 

- Most useful feature of CMOS FPGA is an easy means for general purpose interconnect
- Common method:
  - Grid of metal lines (switching matrix)
  - Junctions = network of pass transistors
  - North, South, East, or West movement
- Pass transistors in CMOS allow current (information) to flow between  $a$  and  $b$
- But in QCA information is moved by *nearness*, not  $e^-$  flow
- No way for pass transistor of only QCA devices

 


Pass Transistor







## The QCA Clock and Pass Transistors

 

- The *relax* clock phase may be the key to the QCA “pass transistor”
- In the *relax* phase QCA cells remain unpolarized so they don’t influence computation
- Pass-transistor-esq routing may be accomplished by using the clock to selectively “turn off” groups of QCA cells to create switches
- Interestingly, a similar technique may be useful to store data
  - However, the *hold* phase would be used to keep data local

 

## Logic Block Candidates

 


- 3 basic logic blocks considered for initial QCA FPGA:
  - A block with a single NAND or NOR gate
  - A block with a programmable majority gate (AND/OR)
  - A block with some form of memory and logic
- Programmable majority gate = sea of AND/OR gates – but no functionally complete logic block!
- Block with memory is nice too – but with it (and option 2) programming signal must be routed/stored
- Basic NAND gate logic block chosen:
  - Its functionally complete
  - Data routing handles all programming
  - This is first cut so let’s keep it simple, huh?








# An Introduction to Interconnect

 

- Again, in CMOS we usually use SRAM memory to configure pass transistors
  - But in QCA there are no pass transistors...at least that can be made exclusively of QCA devices...
  - ...and we're a long way away from a physical SRAM...
  - ...and we want design simplicity
- What about multiplexors?
  - They might offer the most direct translation of CMOS routing techniques to QCA
  - Simple 2x1 multiplexor/1x2 selector could be a pass transistor



# Multiplexors – and why they're bad

   


- Multiplexors require would take at least 6 majority gates!
  - This is much bigger than the NAND gate logic block!!!
- Also, programming signals would have to be stored/routed






# Routing Element Choices

 


## 1 clock zone routing element

 

- ✓ 1 clock zone element allows 2 signals to cross...
- ✓ ...but is ineffective as a routing element as signals cannot be conditionally directed

## A 2x2 zone routing element

 


- ✓ Additional wire segment can be clocked or unclocked
- ✓ Allows for perpendicular crossing or a “corner turn”
- ✓ Problem: signal collision




University of Notre Dame



# Routing Element Choices

 


## A 3x3 zone routing element

 

- ✓ Can alleviate “signal collision” with unclocked zone/buffer
- ✓ Allows increased routing flexibility
- ✓ Problem: area increases by 125%

## A 3x2 zone routing element

 

- ✓ A compromise b/t the 2x2 and 3x3 routing element
- ✓ Allows flexible routing options, a reasonable size, and no signal collisions




University of Notre Dame







## A Complete QCA FPGA

 

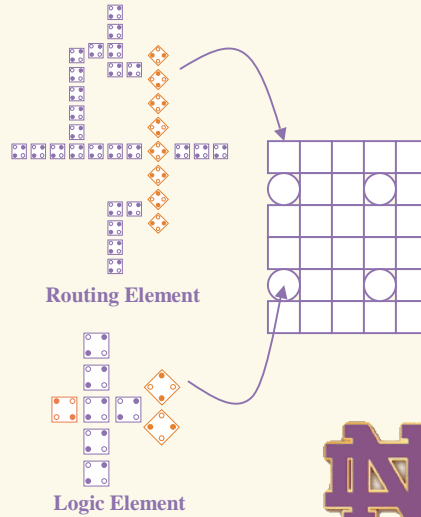
- Routing and logic elements previously discussed are modular – can easily be connected to form complete FPGAs
- CMOS place and routing techniques should still be applicable
- For a physical device:
  - Logic element would probably be scaled to the routing element size
  - Routing element might be scaled to minimum clocking zone width size




## A NAND Adder

 


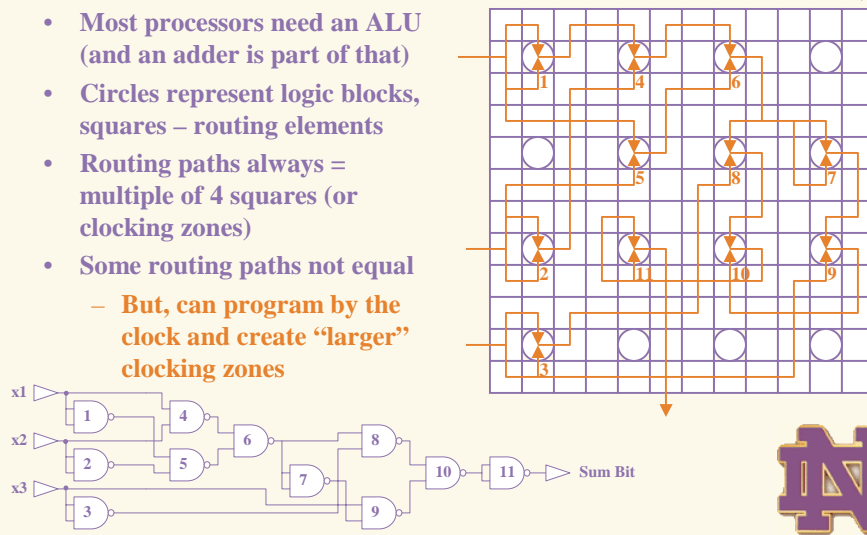
- Most processors need an ALU (and an adder is part of that)
- Circles represent logic blocks, squares – routing elements
- Routing paths always = multiple of 4 squares (or clocking zones)
- Some routing paths not equal
  - But, can program by the clock and create “larger” clocking zones



 
  
## Conclusions

- 1<sup>st</sup> QCA-based FPGA designed
- Circuit components are simple, regular
  - Good candidates for future experimental work
- Potential schemes for implementing QCA switches have been devised
- While our FPGA is simple...
  - Placing and routing is possible
  - Programming sophisticated circuits is possible



## Future Work

- Logical completeness not the only requirement for a “useful” FPGA
  - The ability to store state would also help
- Lack of direct QCA flip-flop equivalent makes this difficult
  - But, data could be stored by creating/programming a QCA wire loop
- Work should continue with the technologists to move to the implementable
- Continue work with “QCA pass transistor”
  - Is there another way to create a similar element?
  - Might it be useful in other applications?

