


# UNIT 8B

## Computer Organization: Levels of Abstraction

15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

1

## A Full Adder

 


A	B	$C_{in}$	$C_{out}$	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

2

# A Full Adder

 

A	B	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = ((A \oplus B) \wedge C) \vee (A \wedge B)$$

15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

3

# Full Adder (FA)

  


15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

4
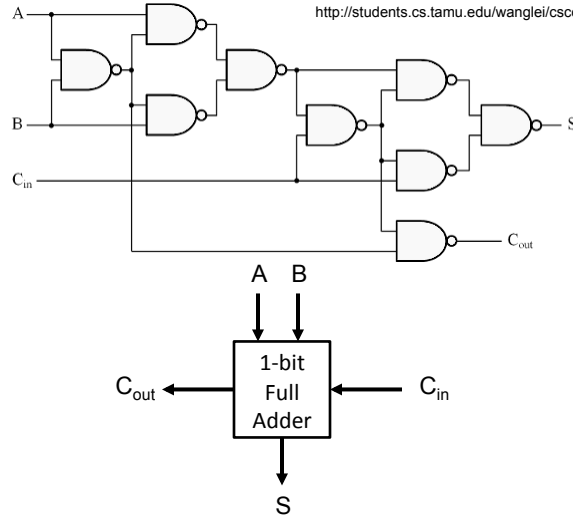
# Another Full Adder (FA)


<http://students.cs.tamu.edu/wanglei/csce350/handout/lab6.html>



15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

5

# 8-bit Full Adder

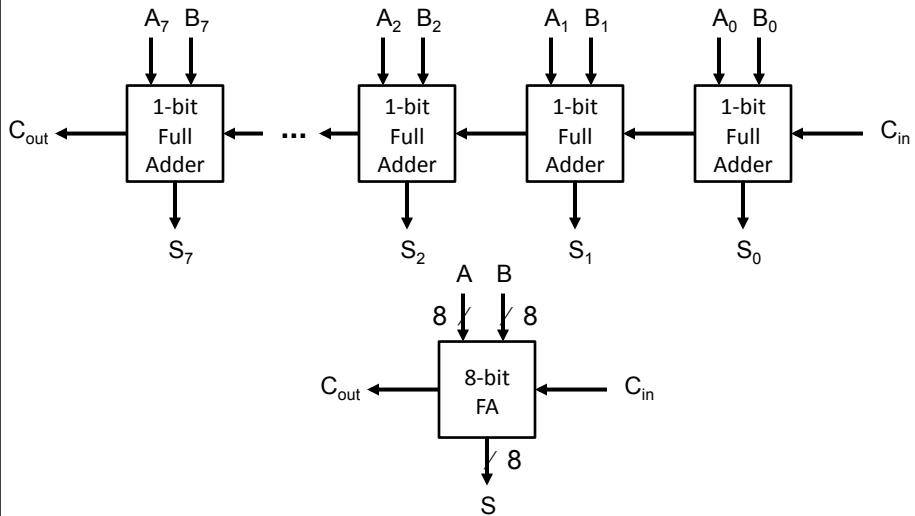


15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

6
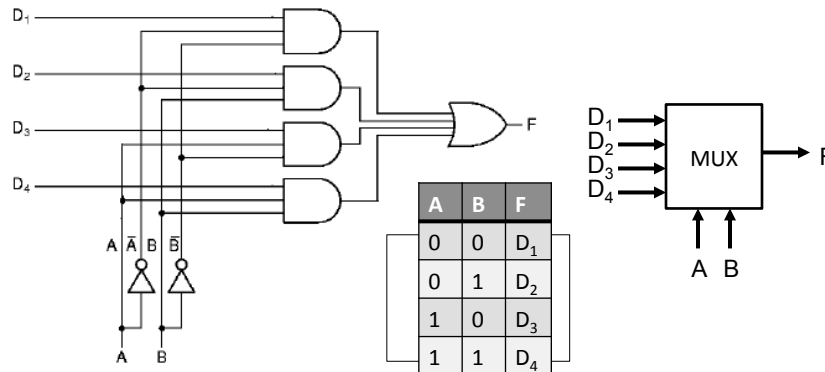
# Multiplexer (MUX)

- A multiplexer chooses between a set of inputs.




<http://www.cise.ufl.edu/~mssz/CompOrg/CDAintro.html>

15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

7

# Arithmetic Logic Unit (ALU)

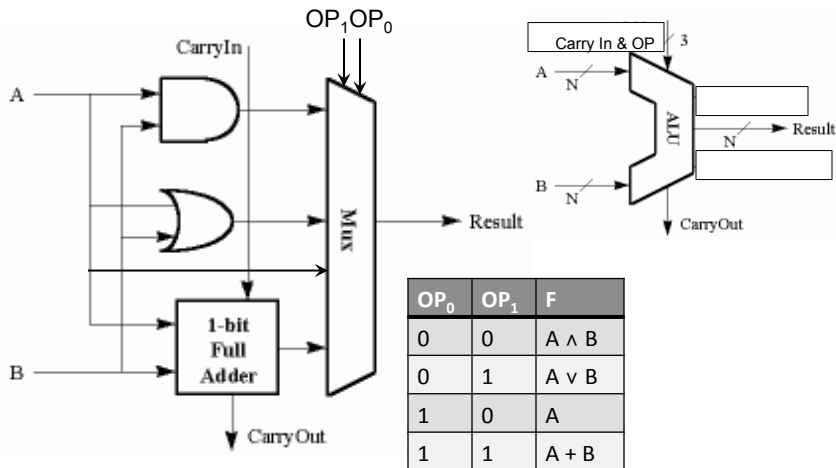


<http://cs-alb-pc3.massey.ac.nz/notes/59304/4.html>

15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

8
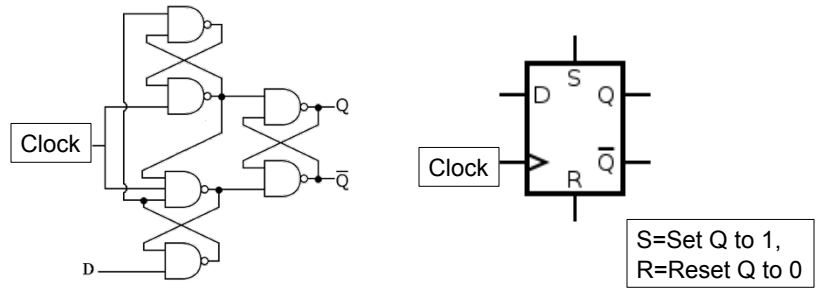
# Flip Flop

- A flip flop is a sequential circuit that is able to maintain (save) a state.
  - Example: D (Data) Flip-Flop – sets output Q to input D when clock turns on. (Images from Wikipedia)




15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

9
 
# Registers

- A register is just a set of edge-triggered flip-flops. Registers are triggered by a clock signal.



<http://cpuville.com/register.htm>


15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

10

# Central Processing Unit (CPU)

- A CPU contains:
  - Arithmetic Logic Unit to perform computation
  - Registers to hold information
    - Instruction register (current instruction being executed)
    - Program counter (to hold location of next instruction in memory)
    - Accumulator (to hold computation result from ALU)
    - Data register(s) (to hold other important data for future use)
  - Control unit to regulate flow of information and operations that are performed at each instruction step


## A sample CPU

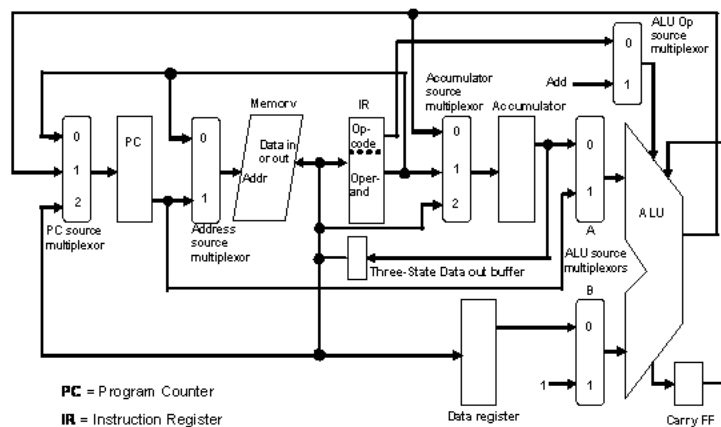

PC = Program Counter  
IR = Instruction Register

<http://cpuville.com/main.htm>

# Computer

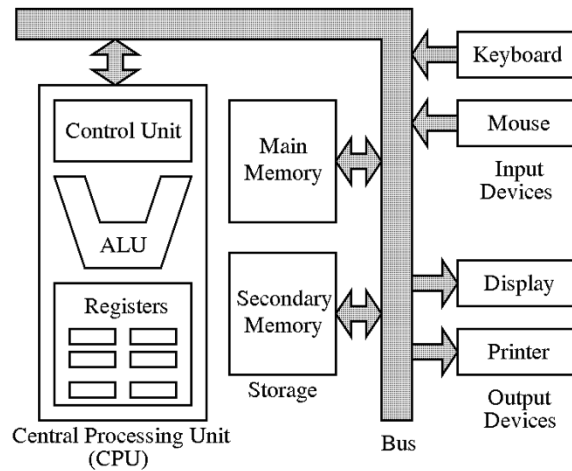

<http://cse.iitkgp.ac.in/pds/notes/intro.html>

15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

13

## Abstraction

- We can use layers of abstraction to hide details of the computer design.
- We can work in any layer, not needing to know how the lower layers work or how the current layer fits into the larger system.
  - > transistors
  - > gates
  - > circuits (adders, multiplexors, flip-flops)
  - > central processing units (ALU, registers, control)
  - > computer

15110 Principles of Computing,  
Carnegie Mellon University - CORTINA

14

## von Neumann Architecture

- Most computers follow the **fetch-decode-execute** cycle introduced by John von Neumann.
  - Fetch next instruction from memory.
  - Decode instruction and get any data it needs (possibly from memory).
  - Execute instruction with data and store results (possibly into memory).
  - Repeat.

## Programming a Machine

- All instructions for a program are stored in computer memory in binary, just like data.
- A program is needed that translates human readable instructions (e.g. in Ruby) into binary instructions (“machine language”).
  - An interpreter is a program that translates one instruction at a time into machine language to be executed by the computer.
  - A compiler is a program that translates an entire program into machine language which is then executed by the computer.